

1 (a) Complete the truth table for the logic expression:


$$X = (A \text{ XOR } B) \text{ NAND } (A \text{ AND } (B \text{ XOR } C))$$

| A | B | C | Working space | X |
|---|---|---|---------------|---|
| 0 | 0 | 0 | | |
| 0 | 0 | 1 | | |
| 0 | 1 | 0 | | |
| 0 | 1 | 1 | | |
| 1 | 0 | 0 | | |
| 1 | 0 | 1 | | |
| 1 | 1 | 0 | | |
| 1 | 1 | 1 | | |

[2]

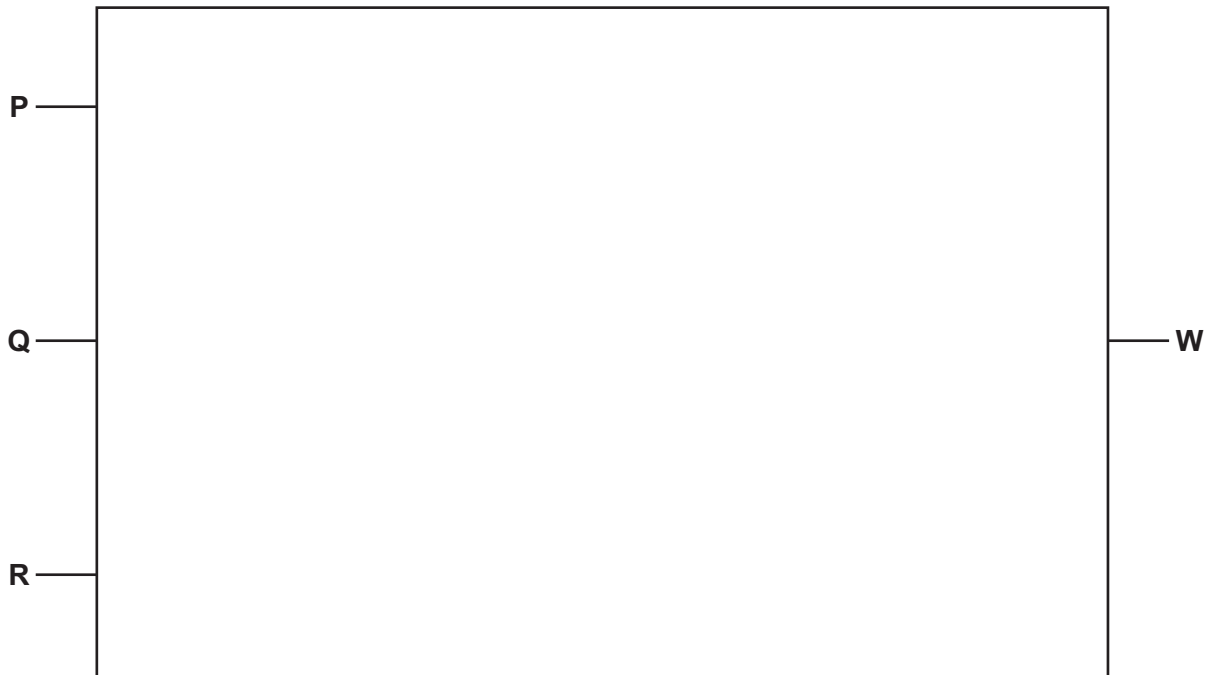(b) Draw the logic circuit for the logic expression:

$$W = P \text{ NAND } ((Q \text{ OR NOT } R) \text{ XOR } (P \text{ XOR } Q))$$



[2]